

Problem Sheet 9

1.

What thermal noise voltage do you expect from a $1\text{ M}\Omega$ resistor measured at room temperature with an instrument which has a 1 kHz bandwidth?

2. SEMINAR PROBLEM I

(a) If 100 V is applied to a forward-biased diode in series with a $10\text{ }\Omega$ resistor, how much shot noise is generated when measured with an instrument of bandwidth 100 kHz ?

(b) If the shot noise signal in (a) is taken across the resistor (i.e. as a voltage) and amplified with an amplifier of gain 10^5 , what will be the voltage noise at the amplifier output? (Assume that the amplifier is 'ideal' and AC-coupled to the resistor)


(c) At room temperature, what will be the thermal noise at the output of the amplifier?

3.

(a) The current from a vacuum tube sensor (e.g. a PMT) is converted to a voltage across a resistor and buffered with a voltage follower. The system has minimal flicker noise, and the amplifier used has a noise factor $F = 1$. What does this value of noise factor mean for the performance of the amplifier, and is it physically achievable in a real device?

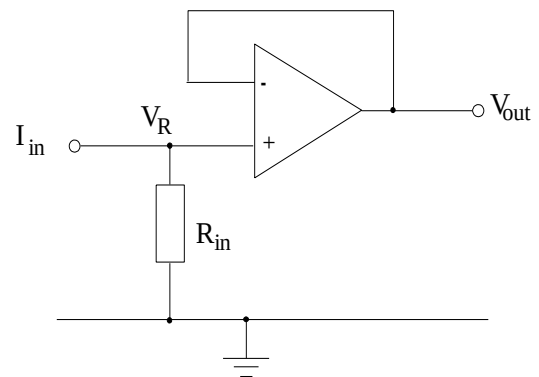(b) Show that the RMS noise voltage at V_{out} is dominated by shot rather than thermal noise for a voltage V_R across R_{in} greater than $2k_B T/e$.

(k_B is Boltzmann's constant, T the temperature in K, and e the electronic charge).



4. SEMINAR PROBLEM II

(a) A $10\text{ k}\Omega$ resistor R_{in} forms the input impedance of an instrument that consists of an input stage with an amplifier of noise factor $F = 4$. The gain of the amplifier stage is a near constant from 100 Hz to 100 kHz , and falls abruptly beyond these points. Assuming thermal noise dominates, what current must flow through the resistor to give a signal to noise ratio of 20 dB at the output with R_{in} initially at 25°C ?

(b) To what temperature must R_{in} be cooled to in order to improve the SNR to 40 dB ?

5.

(a) In flicker noise, what value does the noise power per Hz approach as the frequency f of a measurement approach zero? Why as a result of this are we **not** immediately swamped by flicker noise every time we carry out a DC measurement?

(b) Two identical DC coupled amplifiers with 10 kHz upper frequency limits have been on for 1 and 100 days, respectively. What is the ratio of flicker noise power in the output of these two units?

Instrumentation

Numerical Answers

1 about $4\mu\text{V}$ RMS

2 (a) $0.56\mu\text{A}$ RMS (b) $0.56\text{V}_{\text{RMS}}$ (c) $0.01\text{V}_{\text{RMS}}$

4 (a) $8.2\text{nA}_{\text{RMS}}$ (b) 3K

5 (b) 1.22